 




Stack


demo en el video

iteración n-2




https://drive.google.com/drive/folders/1EYcnWcQHsoRjl-fqdlvCv_UEOs6X6nkv?usp=drive_link

iteración n-1

 

iteración n

 

Single-Cycle Impl.


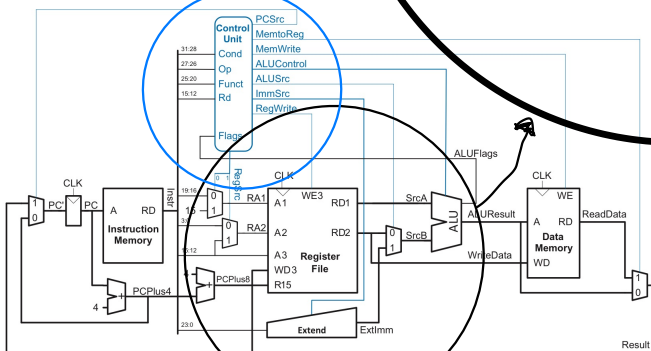
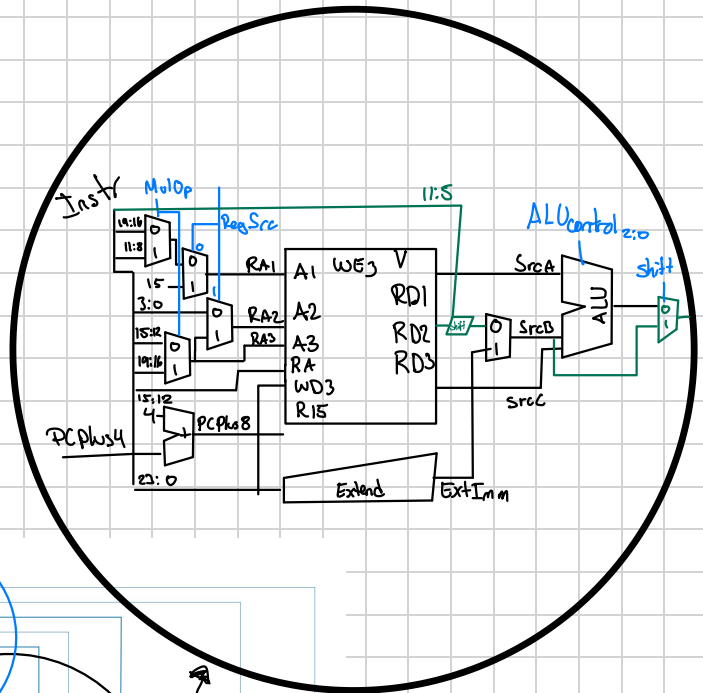
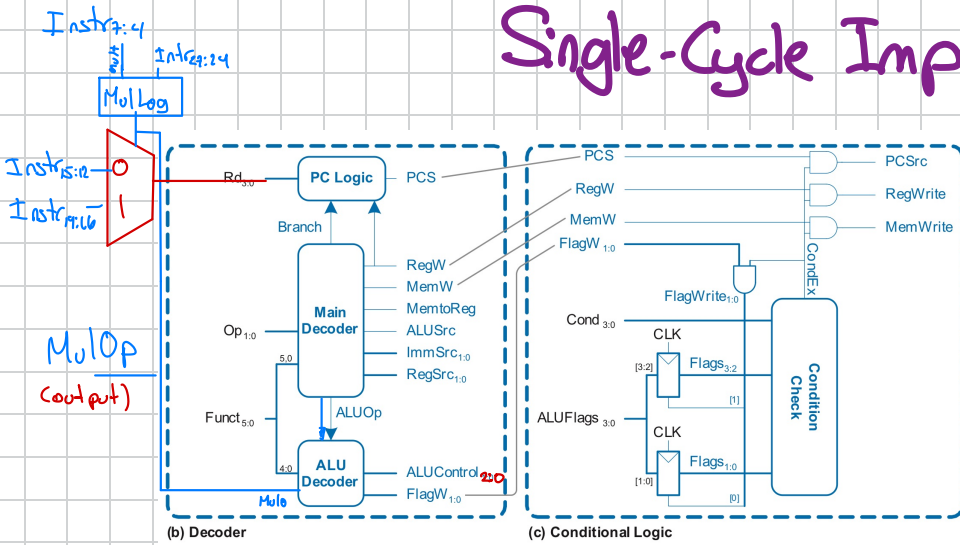


Figure 7.13 Complete single-cycle processor

ALU:

 


MUL Logic:

Inst 7:4 Inst 27:24
A 1 B

MUL Logic

MULOP

$$\sim B \& A == 1001$$

 

Control DIV/MUL

 
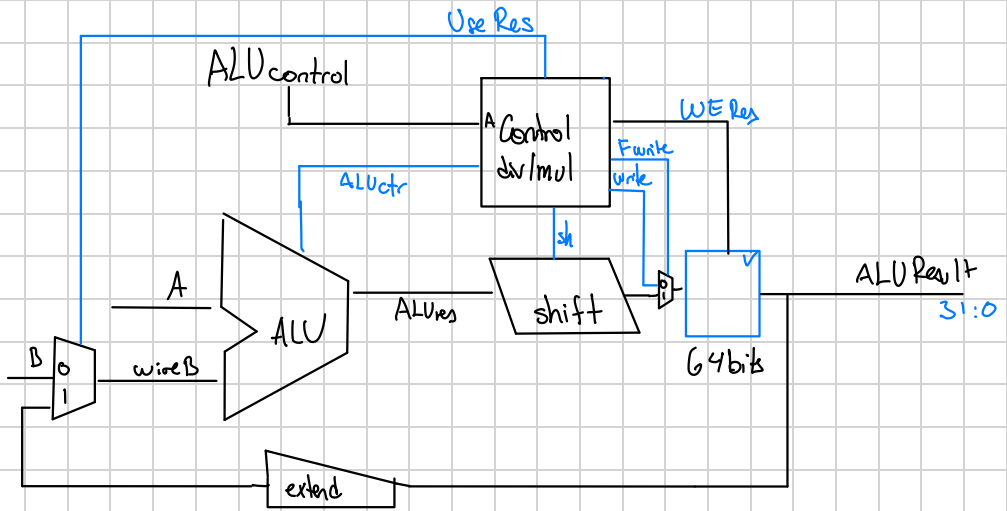


FIGURE 3.11 An improved version of the division hardware. The Divisor register, ALU, and Quotient register are all 32 bits wide, with only the Remainder register left at 64 bits. Compared to Figure 3.8, the ALU and Divisor registers are halved and the remainder is shifted left. This version also combines the Quotient register with the right half of the Remainder register. (As in Figure 3.5, the Remainder register should really be 65 bits to make sure the carry out of the adder is not lost.)

 


FIGURE 3.5 Refined version of the multiplication hardware. Compare with the first version in Figure 3.3. The Multiplicand register, ALU, and Multiplier register are all 32 bits wide, with only the Product register left at 64 bits. Now the product is shifted right. The separate Multiplier register also disappeared. The multiplier is placed instead in the right half of the Product register. These changes are highlighted in color. (The Product register should really be 65 bits to hold the carry out of the adder, but it's shown here as 64 bits to highlight the evolution from Figure 3.3.)

Patterson, D. A., & Hennessy, J. L. (2016). Computer Organization and Design ARM Edition: The Hardware Software Interface. Morgan Kaufmann.



Recuperado de:
(bibliografía
complementaria del
curso)

CMD

001	MLA
100	SDIV
110	UDIV

↓ ↓
 divide accumulate

Implementación Multi-cycle

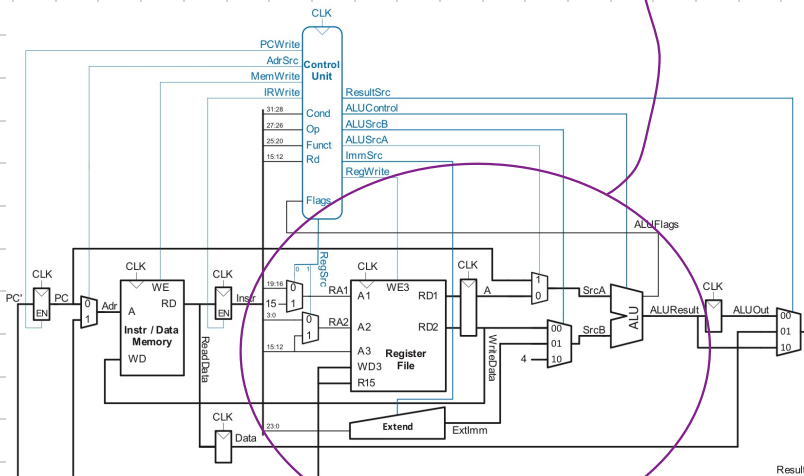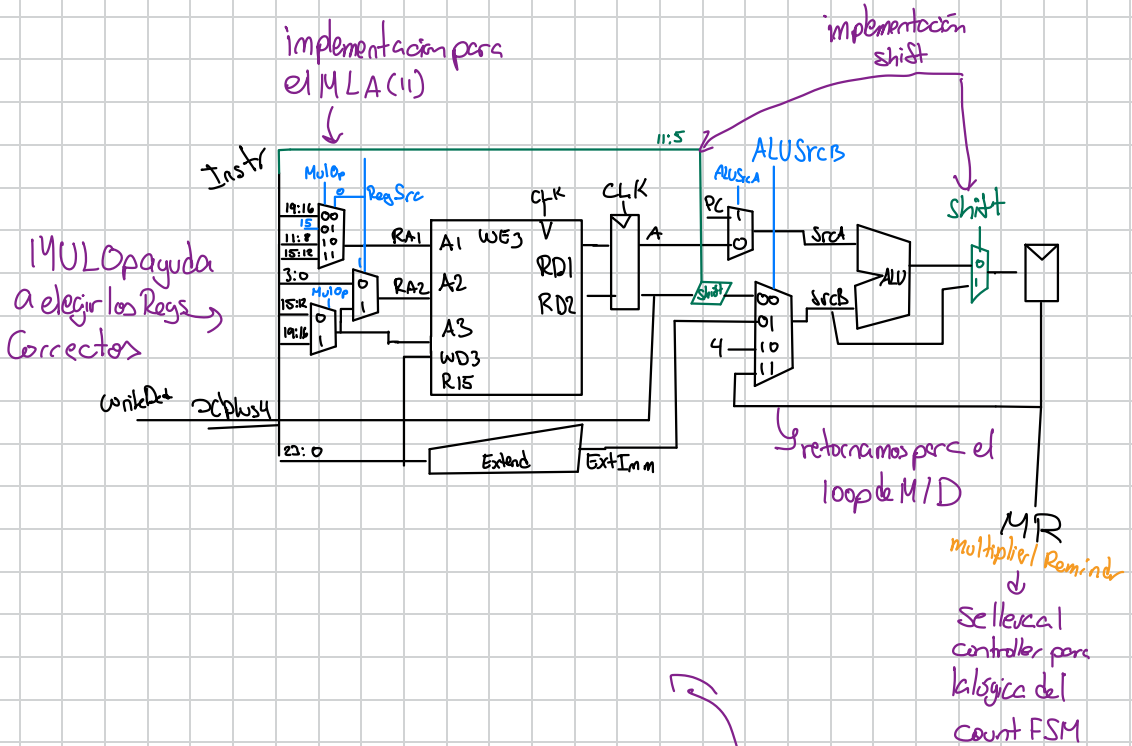


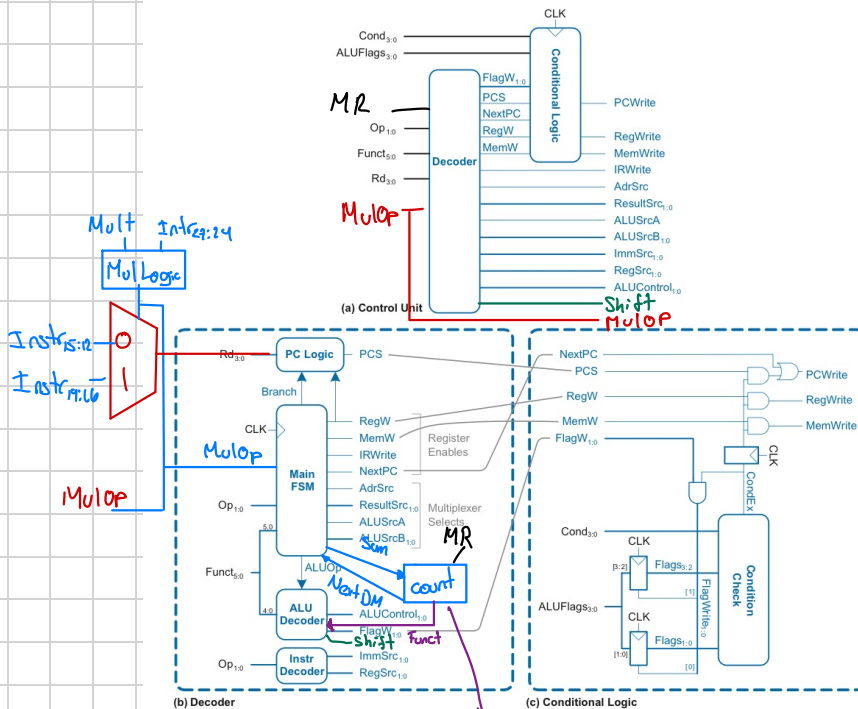


Figure 7-31 Multicycle control unit

FSM control

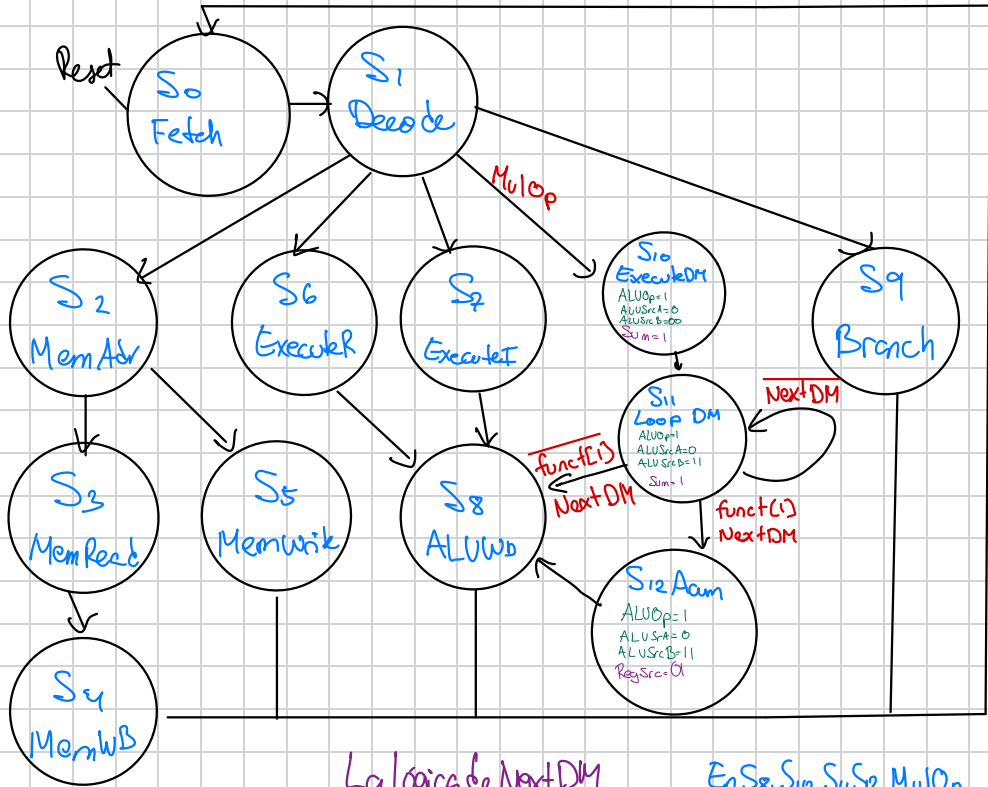

S10: ingresa contenido de ambos registros
 S11: empieza a tomar en SrcB, el anterior valor, Src A queda su valor anterior

S12: en caso se necesite MLA, se toma el RA y se suma la multiplicación obtenida

State (Name)	NextPC	Branch	MemW	RegW	IRWrite	AddrSrc	ResultSrc	ALUSrcA	ALUSrcB	ALUOp	Sum
0 (Fetch)	1	0	0	0	1	0	10	0	1	10	0
1 (Decode)	0	0	0	0	0	0	10	0	1	10	0
2 (MemAdr)	0	0	0	0	0	0	00	0	0	01	0
3 (MemRead)	0	0	0	0	0	1	00	0	0	00	0
4 (MemWB)	0	0	0	1	0	0	01	0	0	00	0
5 (MemWrite)	0	0	1	0	0	1	00	0	0	00	0
6 (ExecuteR)	0	0	0	0	0	0	00	0	0	00	1
7 (ExecuteI)	0	0	0	0	0	0	00	0	0	01	1
8 (ALUWB)	0	0	0	1	0	0	00	0	0	00	0
9 (Branch)	0	1	0	0	0	0	10	1	0	01	0
10 (ExecuteDM)	0	0	0	0	0	0	00	0	0	00	1
11 (LoopDM)	0	0	0	0	0	0	00	0	0	11	1
12 (Mcum)	0	0	0	0	0	0	01	0	0	11	1

Count FSM




FSM que toma la lógica de MLA, SDIV, UDIV

CMD

001	MLA
100	SDIV
110	UDIV

↓ divide ↓ accumulate

Diagrama de flujo:

 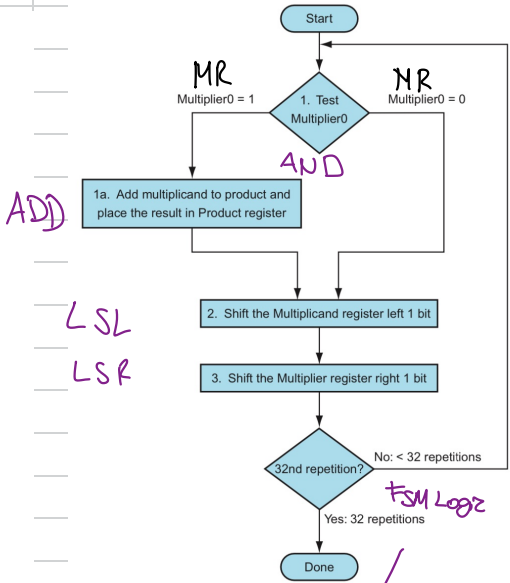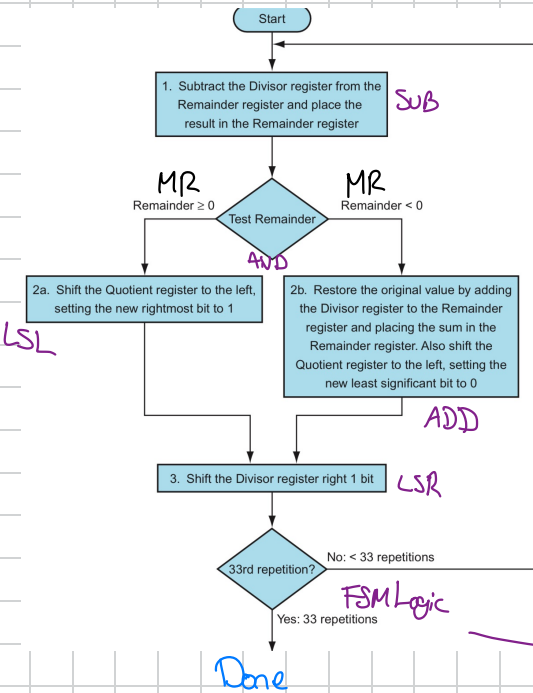

Recuperado de:
(bibliografía
complementaria del
curso)

Patterson, D. A., & Hennessy, J. L. (2016). Computer Organization and Design ARM Edition: The Hardware Software Interface. Morgan Kaufmann.